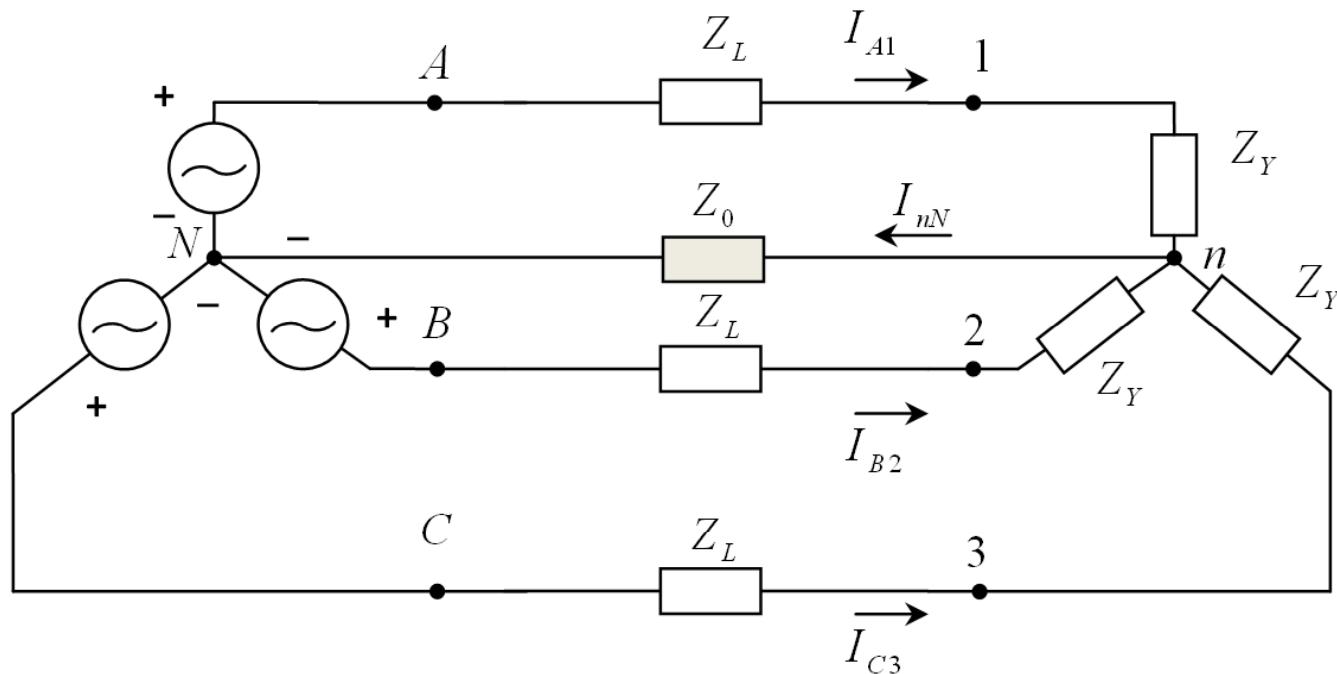


Circuito Trifásico Balanceado


Prof. Gerardo Ceballos

Circuito Trifásico Balanceado

- Generador balanceado
- Z_L iguales para las 3 líneas
- Z_Y ó Z_Δ iguales en la carga



Circuito Trifásico Balanceado

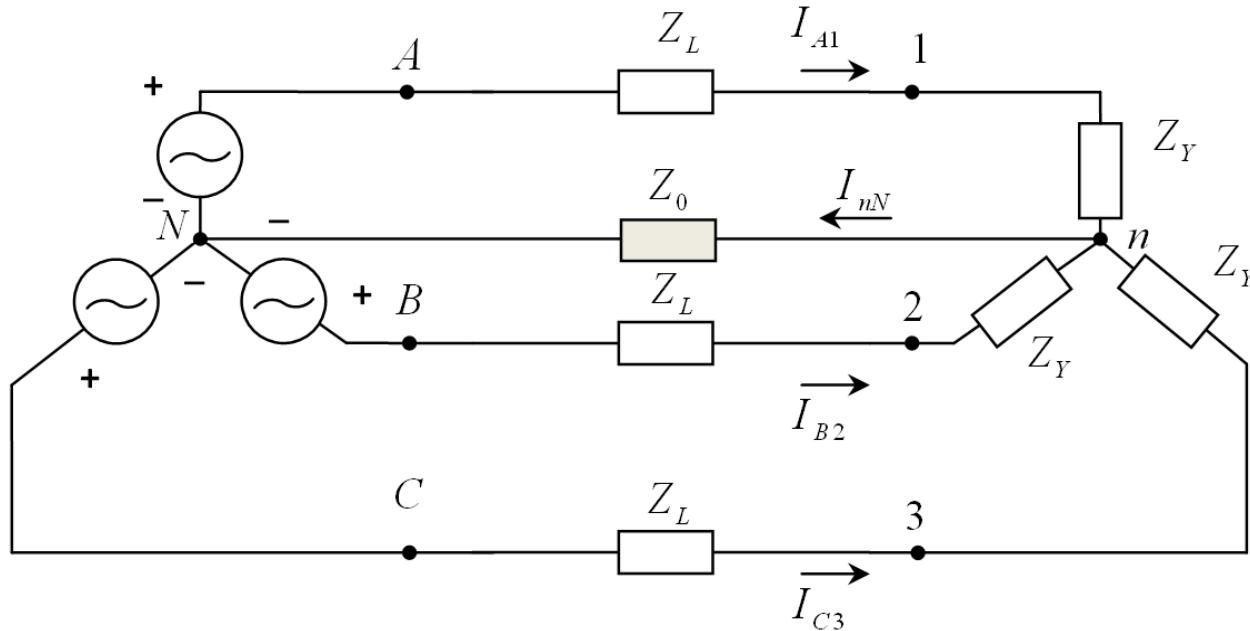

$$I_{nN} = I_{A1} + I_{B2} + I_{C3}$$

$$V_{nN} = 0$$

Z_0 Cualquier valor, 0, ∞


$$I_{nN} = 0$$

$$I_{A1} + I_{B2} + I_{C3} = 0$$

$$\frac{V_{nN}}{Z_0} = \frac{V_{AN} - V_{nN}}{Z_L + Z_Y} + \frac{V_{BN} - V_{nN}}{Z_L + Z_Y} + \frac{V_{CN} - V_{nN}}{Z_L + Z_Y}$$


$$V_{nN} \left(\frac{1}{Z_0} + \frac{3}{Z_L + Z_Y} \right) = \frac{V_{AN} + V_{BN} + V_{CN}}{Z_L + Z_Y} \xrightarrow{0} V_{nN} = 0$$

Circuito Trifásico Balanceado

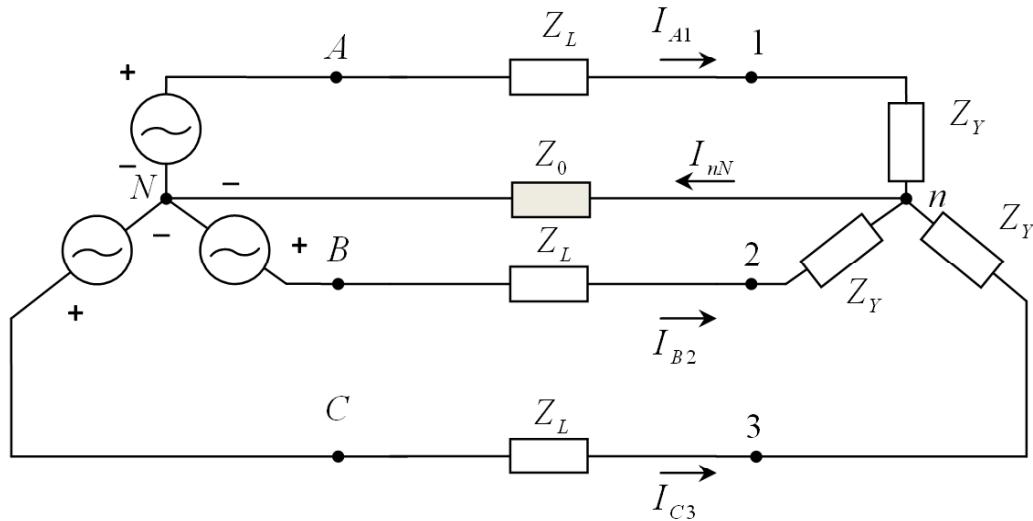


No importa si existe el cable de neutro o no, en el circuito trifásico balanceado $V_{nN}=0$

→ se puede analizar con una sola malla

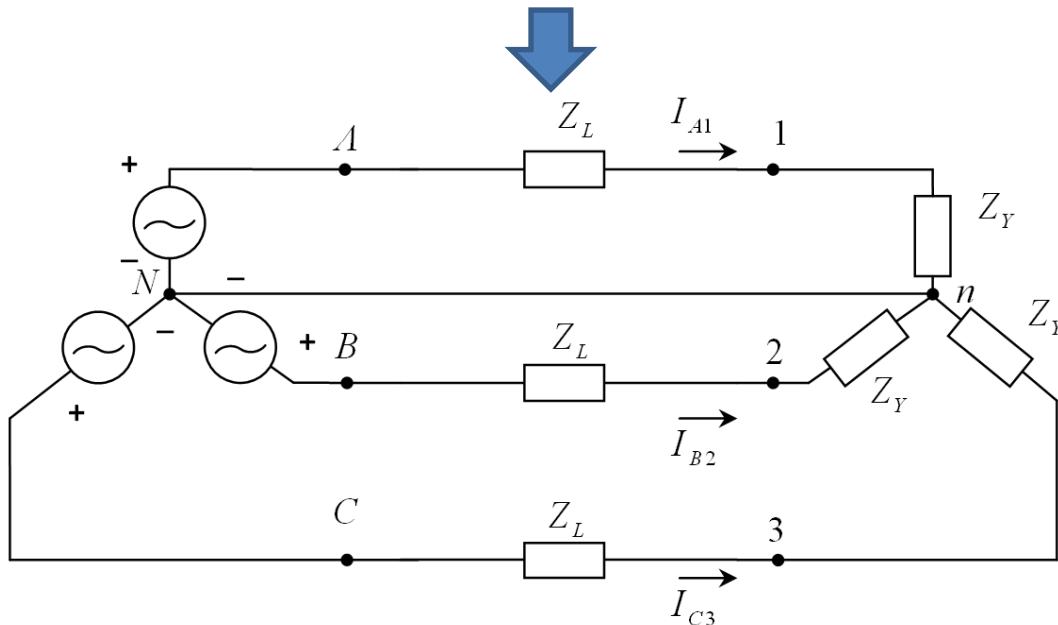


Circuito Trifásico Balanceado


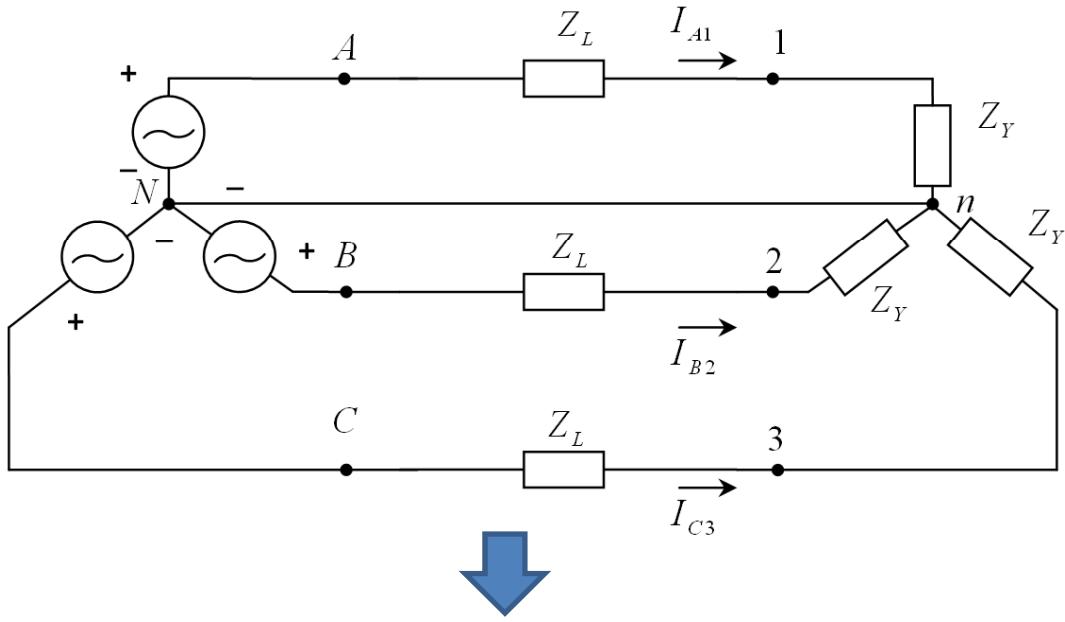


$$I_{A1} = \frac{V_\phi |0^\circ|}{Z_L + Z_Y} = |I_L| |0^\circ|$$

$$I_{B2} = \frac{V_\phi |-120^\circ|}{Z_L + Z_Y} = |I_L| |-120^\circ|$$

$$I_{C3} = \frac{V_\phi |+120^\circ|}{Z_L + Z_Y} = |I_L| |+120^\circ|$$

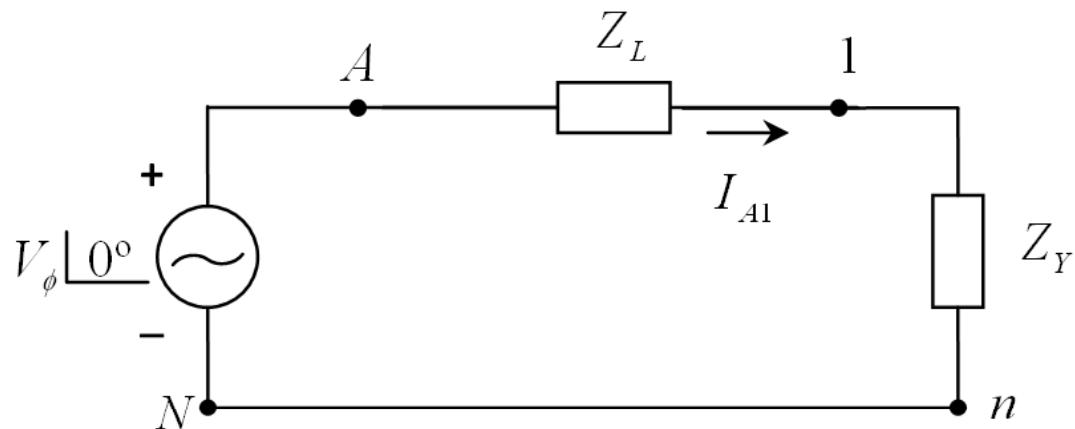

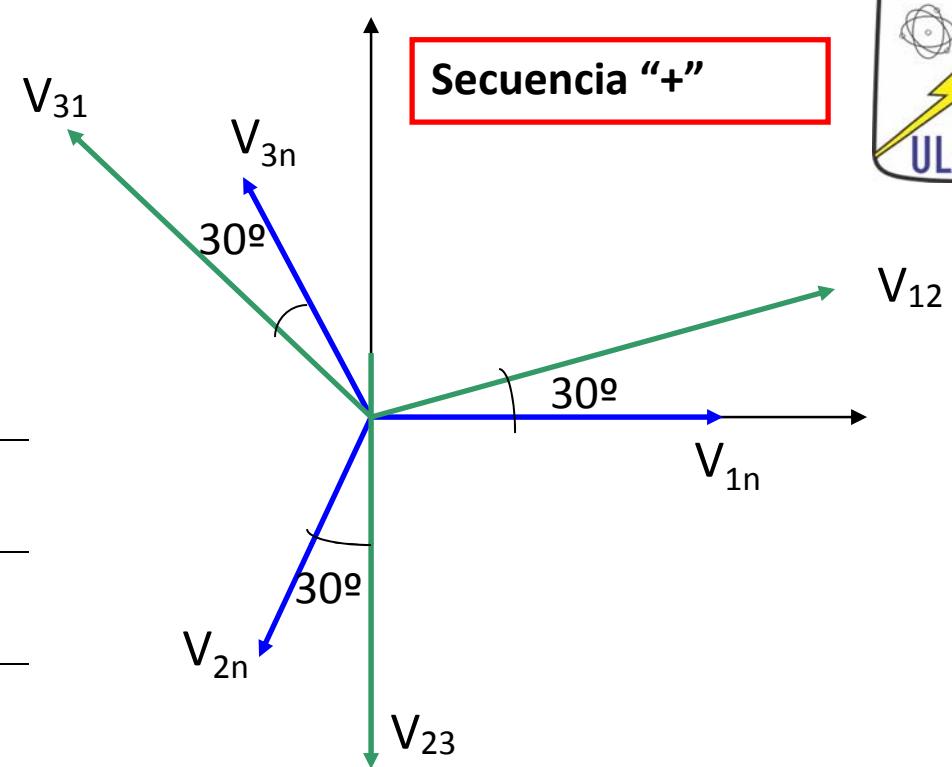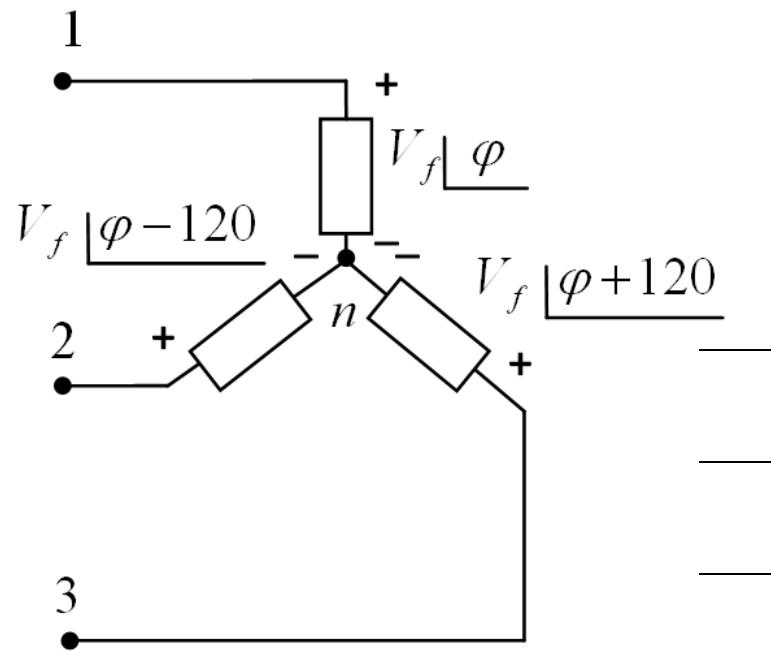

$$V_{12} = \sqrt{3} |V_f| \underline{|\varphi + 30|}$$


$$V_{23} = \sqrt{3} |V_f| \underline{|\varphi - 120 + 30|}$$

$$V_{31} = \sqrt{3} |V_f| \underline{|\varphi + 120 + 30|}$$

$$V_{12} = V_{1n} - V_{2n}$$

Un fasor menos una versión del mismo atrasada en 120°

$\Rightarrow + 30$

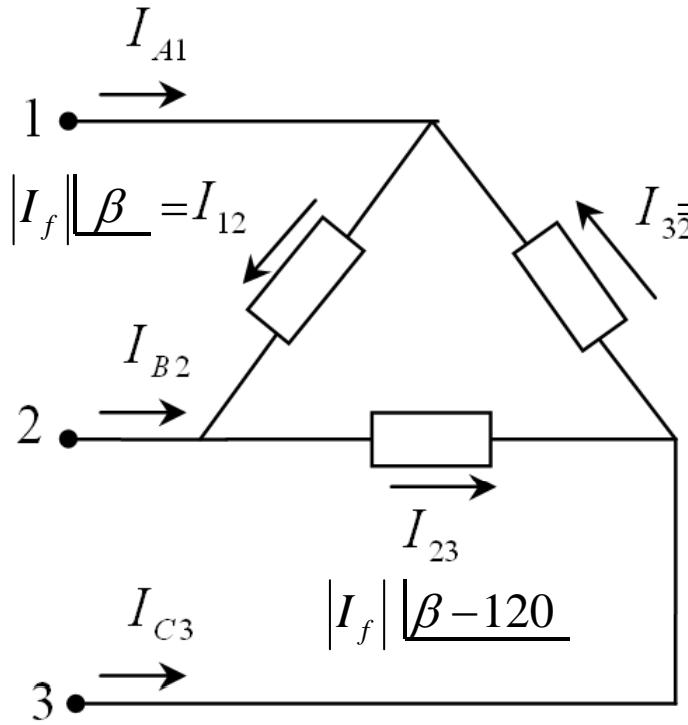


$$I_{A1} = \sqrt{3} |I_f| \beta - 30$$

$$I_{B2} = \sqrt{3} |I_f| \beta - 120 - 30$$



$$I_{C3} = \sqrt{3} |I_f| \beta + 120 - 30$$

$$I_{A1} = I_{12} - I_{31} \rightarrow \text{Un fasor menos una versión del mismo adelantada en } 120^\circ$$

$\rightarrow -30$

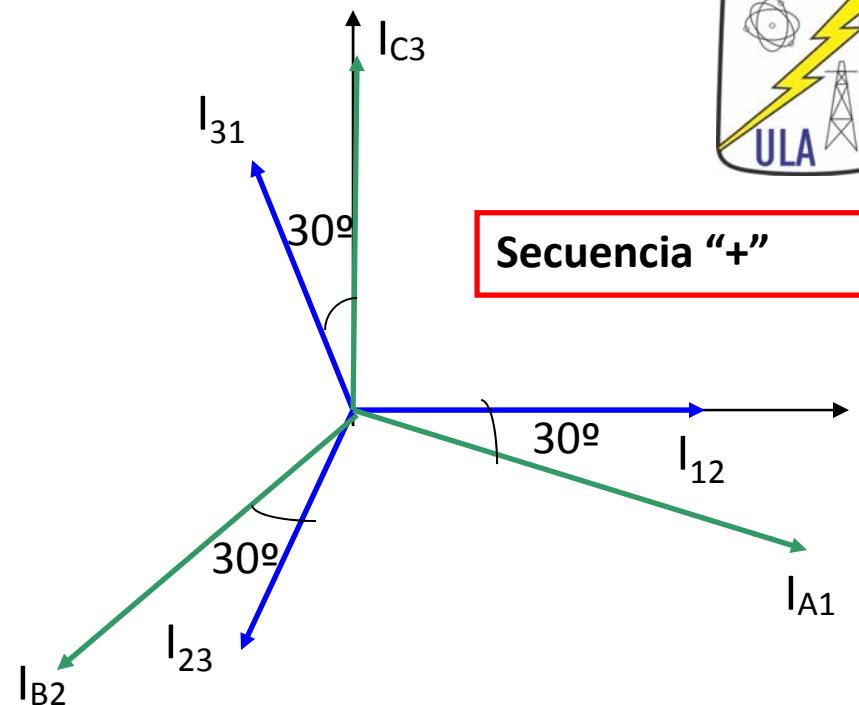

Ejemplo

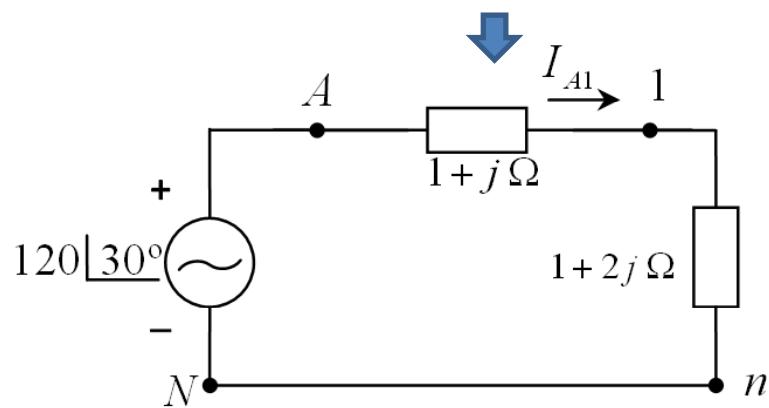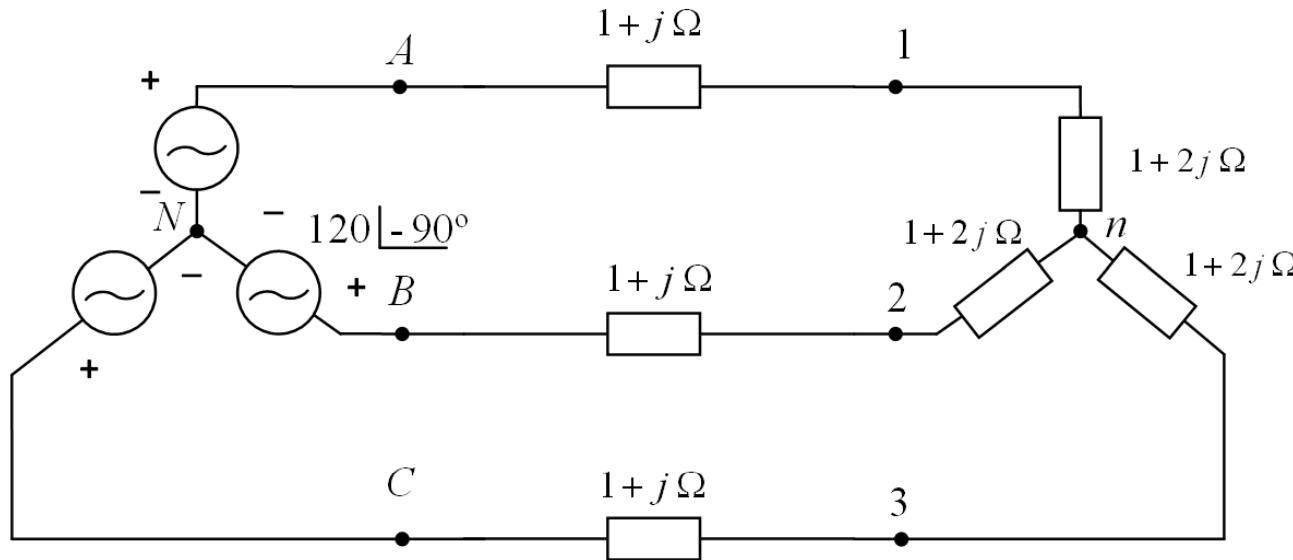

$$I_{A1} = \frac{120\angle 30^\circ}{2 + 3j} = 33,28\angle -26^\circ$$

$$I_{B2} = 33,28\angle -146^\circ$$

$$I_{C3} = 33,28\angle 94^\circ$$

$$V_{1n} = I_{A1}(1 + 2j) = 74,41\angle 37,43^\circ$$

$$V_{12} = \sqrt{3}(74,41)\angle 37,43^\circ + 30^\circ = 128,89\angle 67,43^\circ$$